

Network Analysis

Practice Test I (Solutions)

①

1. $i(t) = 1 - 4e^{-2t} + 3e^{-3t}$. A. for $t \geq 0$.

$$q(t) = \int_{-\infty}^t i(t) dt$$

$$= \int_{-\infty}^0 i(t) dt + \int_0^t i(t) dt$$

$$= 0 + \int_0^t (1 - 4e^{-2t} + 3e^{-3t}) dt$$

$$= (t + 2e^{-2t} - e^{-3t}) \text{ A.C.}$$

Institute of Engineering Studies (IES)

56, 2nd floor, behind Namura Hotel

22nd Main, Marehalli, J.P. Nagar

2nd Phase, Bangalore-560 075

Ph: 080 32491693/0741900225

2. $V = 5000 \text{ V}$.

$$\text{Energy} = (\text{Voltage} \times \text{Charge})$$

$$= (5000 \times 1.602 \times 10^{-19})$$

$$= 8.01 \times 10^{-16} \text{ J}$$

$$\begin{aligned} \therefore e^- &= -1.602 \times 10^{-19} \text{ C} \\ &= -pt \end{aligned}$$

This energy should be stored in the form of Kinetic Energy.

$$\Rightarrow \text{K.E} = \frac{1}{2} m_p v_p^2 = 8.01 \times 10^{-16}$$

$$\Rightarrow v_p^2 = + \sqrt{\frac{8.01 \times 10^{-16} \times 2}{1832 \times 9.11 \times 10^{-31}}}$$

$$\therefore m_e = 9.11 \times 10^{-31} \text{ kg}$$

$$= 979.736 \text{ km/sec} = 7.797 \times 10^5 \text{ m/sec}$$

3. $V = 20 \text{ KV}$.


$$\text{Energy} = (20 \times 10^3 \times 1.602 \times 10^{-19}) \text{ J}$$

$$= 3.204 \times 10^{-15} \text{ J}$$

$$\Rightarrow \text{K.E} = \frac{1}{2} m_e v_e^2 = 3.204 \times 10^{-15}$$

$$\Rightarrow v_e = + \sqrt{\frac{3.204 \times 10^{-15} \times 2}{9.1066 \times 10^{-31} \text{ kg}}} = 83885 \times 10^6 \text{ m/sec}$$

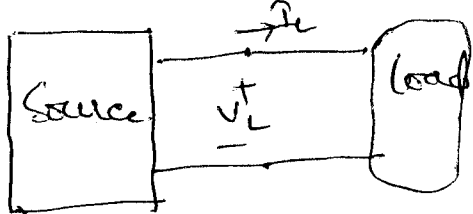4. $V_L = 16 - 4I_L^2$ for $0 \leq I_L \leq 2$
 $= 0$ for $I_L \geq 2$



Power absorbed by load = $(V_L I_L)$

(a) for $I_L = 1A$, $V_L = 16 - 4I_L^2 = 12 \cdot V$



$\Rightarrow P_{ab} = 12 \times 1 = 12W$

(b) for $I_L = 2A$, $V_L = 0 \cdot V$

$\Rightarrow P_{ab} = 0(2) = 0W$

Institute of Engineering Studies (IES)
 # 56, 2nd floor, behind Namura Hotel
 22nd Main, Marenahalli, J.P. Nagar
 2nd Phase, Bangalore-560 076
 Ph: 080 32491693/9741900225

5.

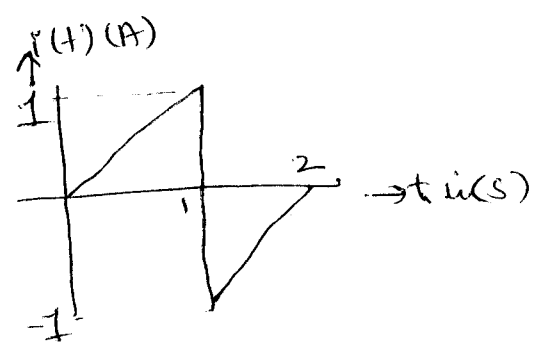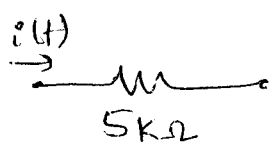

(a) $i(t) = t$ for $0 \leq t \leq 1$

$P(t) = i^2(t) \cdot R$

$= t^2 \cdot (5 \times 10^3) \cdot W$ for $0 \leq t \leq 1$

Energy, $E = \int_{-\infty}^t P(t) dt$

$= \int_{-\infty}^0 P(t) dt + \int_0^t P(t) dt$

$= 0 + \int_0^t 5 \times 10^3 t^2 dt$ for $0 \leq t \leq 1$

$= \left[\frac{5 \times 10^3}{3} t^3 \right]_0^1 = \frac{5 \times 10^3}{3} J$


By symmetry, $E|_0^1 = E|_1^2$

\Rightarrow Total Energy, ~~from~~ for $0 \leq t \leq 2$,

$E = 2 \times E|_0^1 = \frac{2 \times 5 \times 10^3}{3} = \frac{10^4}{3} J$

(b) By symmetry, as Area under $i(t)|_0^1 = \text{Area under } i(t)|_1^2$ ③
 \Rightarrow Total charge transferred = 0. for $0 \leq t \leq 2$.

6.

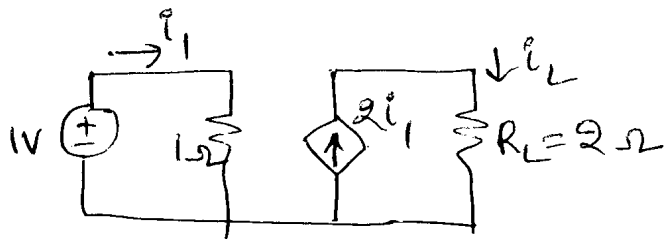

Institute of Engineering Studies (IES)

56, 2nd floor, behind Namura hotel

22nd Main, Marenahalli, J.P. Nagar


2nd Phase, Bangalore-560 078

Ph: 080 32491693/9741900225

$$\Rightarrow i_1 = \frac{1}{1} = 1 \text{ A};$$

$$\Rightarrow i_L = 2i_1 = 2 \text{ A.} \Rightarrow \text{Power absorbed by } R_L = i_L^2 R = 4 \times 2 = 8 \text{ W.}$$

7.

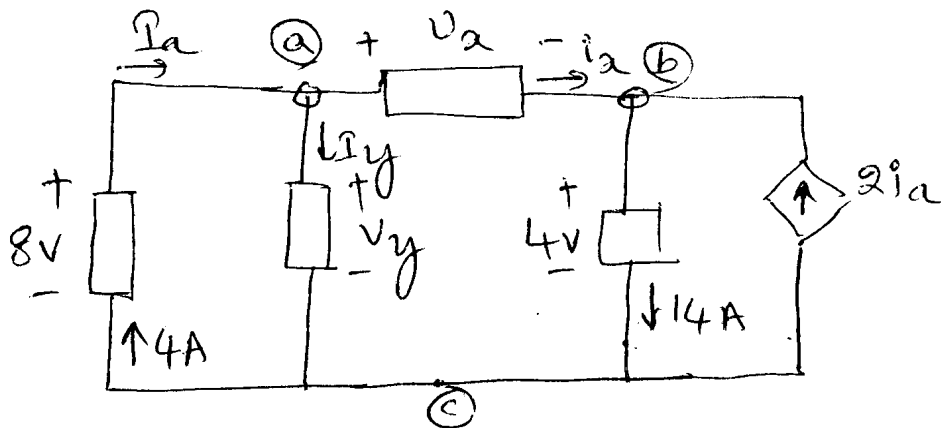

$$I_a = 4 \text{ A}; \Rightarrow 2i_a = 8 \text{ A};$$

By applying KCL @ node b;

$$14 - 2i_a - i_a = 0$$

$$\Rightarrow i_a = -14 + 2i_a$$

$$= -14 + 8 = -6 \text{ A.} \quad \text{--- ①}$$

By applying KCL @ node a;

$$-I_a + I_y + i_a = 0.$$

$$\Rightarrow I_y = I_a - i_a$$

$$= 4 + 6 = 10 \text{ A.} \quad \text{--- ②}$$


By applying KVL thro' 8V element and v_y ,

$$v_y = 8V \quad \text{--- (3)}$$

By applying KVL thro' v_y , v_a and 4V,

$$\begin{aligned} v_a &= v_y - 4 \\ &= 8 - 4 \\ &= 4V \quad \text{--- (4)} \end{aligned}$$

8.

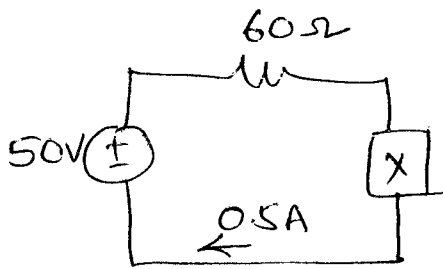

Power delivered by 50V

$$= 50 \times 0.5$$

$$= 25W$$

Power absorbed by 60Ω = $0.5^2 \times 60$


$$= 15W$$

Power absorbed by X = Power delivered by 50V - Power absorbed by 60Ω

$$= 25 - 15$$

$$= 10W$$

9.

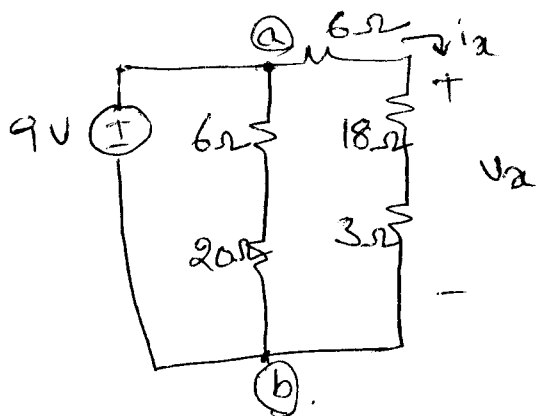

$$i_2 = \frac{9}{(6+18+3)} \cdot A$$

$$= \frac{1}{3} A$$

$$\Rightarrow v_2 = i_2 (18+3)$$

$$= 7V$$

Institute of Engineering Studies (IES)

56, 2nd floor, behind Namura hotel


22nd Main, Marenahalli, J.P. Nagar

2nd Phase, Bangalore-560 078

Ph: 080 32491693/9741900225

10.

(a)

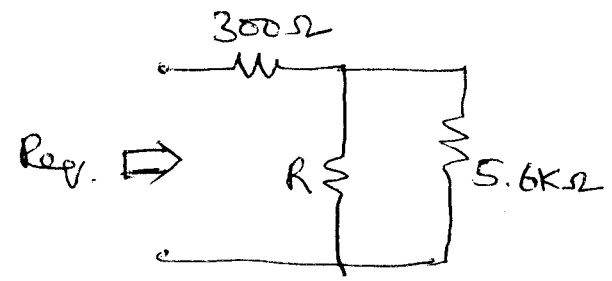


$$R_{eq} = [5.6 \times 10^3 \parallel R] + 300 \quad ; \quad R_{eq} = 1000 \Omega$$

$$700 = \frac{5.6 \times 10^3 \times R}{R + 5.6 \times 10^3}$$

$$\Rightarrow 700R + 700 \times 5.6 \times 10^3 = 5.6 \times 10^3 \times R$$

$$\Rightarrow R = \underline{\underline{800 \Omega}}$$

(b)

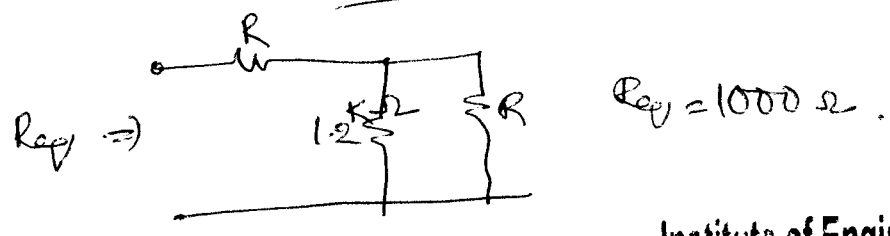

$$R_{eq} = (1.2 \text{ k} \parallel R) + R$$

$$\Rightarrow \frac{1.2 \times 10^3 \times R}{1.2 \times 10^3 + R} + R = 1000$$

$$\Rightarrow R^2 + 2.4 \times 10^3 R - 1000 = 0$$

$$R = \frac{-2.4 \times 10^3 \pm \sqrt{(2.4 \times 10^3)^2 + 4 \times 1000}}{2}$$

$$R^2 + 2.4 \times 10^3 R - 1000(1.2 \times 10^3 + R) = 0$$


$$\Rightarrow R^2 + 1.4 \times 10^3 R - 1.2 \times 10^6 = 0$$

$$\Rightarrow R = \frac{-1.4 \times 10^3 \pm \sqrt{(1.4 \times 10^3)^2 + 4 \times 1.2 \times 10^6}}{2}$$

$$= \left(\frac{-1.4 + 2.6}{2} \right) \times 10^3 = \underline{\underline{600 \Omega}}$$

Institute of Engineering Studies (IES)
 # 56, 2nd floor, behind Namura hotel
 22nd Main, Marenahalli, J.P. Nagar
 2nd Phase, Bangalore-560 078
 Ph: 080 32491693/9741900225

11.

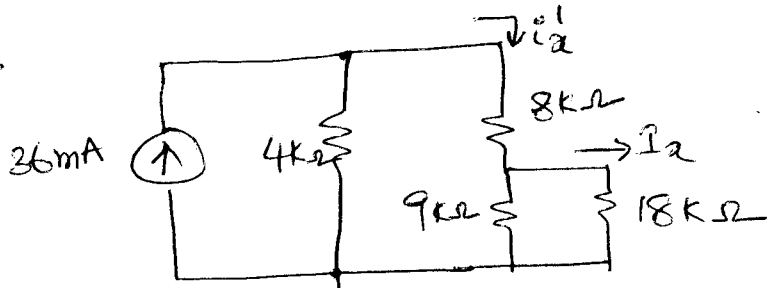

Institute of Engineering Studies (IES)

56, 2nd floor, behind Namura hotel,
22nd Main, Marenahalli, J.P. Nagar
2nd Phase, Bangalore-560 078
Ph: 080 32491693/9741900225

Combination of $8k\Omega$, $9k\Omega$ & $18k\Omega$ will give

$$(9k \parallel 18k) + 8k = \left(\frac{9 \times 18}{9 + 18} + 8 \right) \cdot k\Omega$$

$$= 14k\Omega$$


By current Division Rule,

$$i_a' = \frac{36 \times 10^{-3} \times 4 \times 10^3}{(4 \times 10^3 + 14 \times 10^3)} = 8mA$$

Again by current Division rule,

$$I_a = i_a' \left(\frac{9}{9 + 18} \right) = 8 \left(\frac{9}{27} \right) = \underline{\underline{\frac{8}{3} mA}}$$

12.

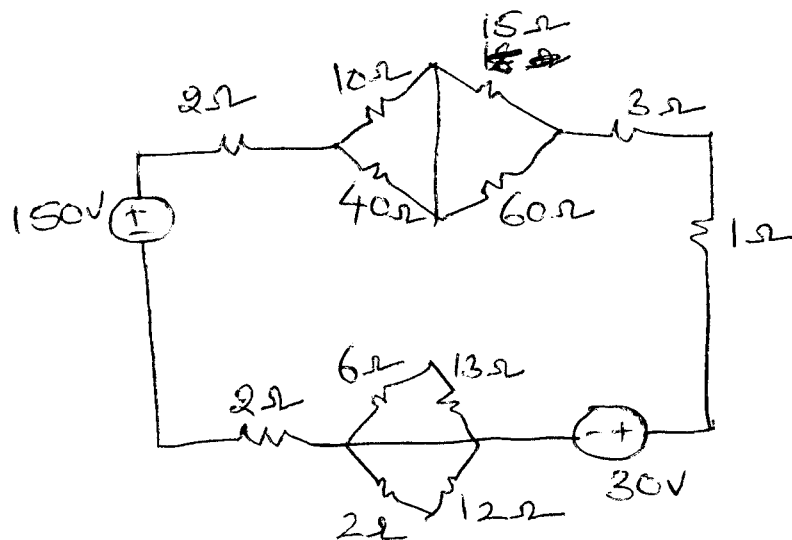

Combination of 6Ω , 13Ω , 2Ω & 12Ω need not be considered as they are short circuited.

parallel combination of 10Ω , 15Ω , 40Ω & 60Ω will give


$$(10 \parallel 40 + 15 \parallel 60) \Omega = \frac{10 \times 40}{10 + 40} + \frac{15 \times 60}{15 + 60}$$

$$= 8 + 12$$

$$= 20 \Omega$$

After source combination of 150V & 30V will give
 $150 - 30 = 120V$.

⇒ circuit will become.

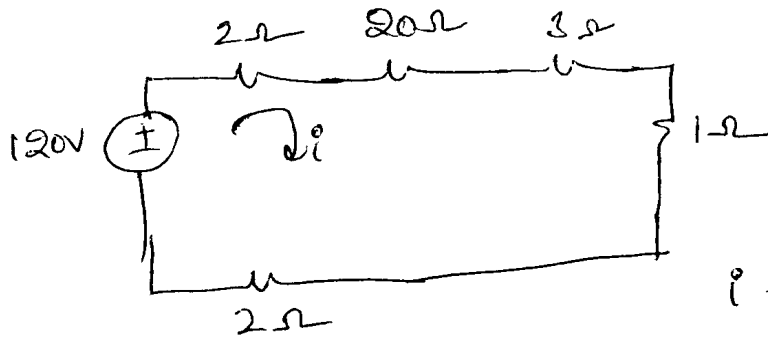

$$i = \frac{120}{28}$$

$$= \frac{30}{7} \text{ A}$$

⇒ Power absorbed by $10\Omega = i^2 \times R$

$$= \left(\frac{30}{7}\right)^2 \times 1 = \frac{900}{49} \text{ W}$$

By current Division, current flowing thro' 10Ω ,

$$= i \times \frac{40}{10+40} = \frac{24}{7} \text{ A}$$

Power absorbed by $10\Omega = \left(\frac{24}{7}\right)^2 \times 10$

$$= \underline{\underline{1.17 \text{ kW}}}$$

Power absorbed by $13\Omega = 0$ [∵ No current is flowing thro']

Institute of Engineering Studies (IES)

56, 2nd floor, behind Namura hotel

22nd Main, Marenahalli, J.P. Nagar

2nd Phase, Bangalore-560 078

Ph: 080 32491693/9741900225

13.

$$\begin{array}{c} \rightarrow i \\ \text{---} \text{---} \text{---} \text{---} \\ + \quad V \quad - \end{array} \quad i = 80t e^{-100t} \text{ m.A. for } t > 0.$$

$$L = 50 \text{ mH.}$$

to find $t_{i_{\max}}$

$$i(t) = 80t e^{-100t} \text{ m.A.}$$

$$\frac{di(t)}{dt} = 80 e^{-100t} - 8000t e^{-100t} = 0.$$

$$\Rightarrow t = 0.01 \text{ sec.}$$

$$\Rightarrow t$$

$$\Rightarrow t_{i_{\max}} = 0.01 \text{ sec}$$

$$\Rightarrow I_{\max} = 80t e^{-100t} \Big|_{t=0.01} = 0.2943 \text{ A.}$$

to find $t_{V_{\max}}$

$$v(t) = L \frac{di}{dt}$$

$$= 50 \times 10^{-3} (80 e^{-100t} - 8000t e^{-100t})$$

$$\frac{dv(t)}{dt} \Big|_{t_{V_{\max}}} = 0.$$

$$\Rightarrow -100 e^{-100t} - 100 (-10000t e^{-100t}) = 0$$

$$\Rightarrow -1 + (1 - 100t) = 0.$$



$$\Rightarrow t = \frac{2}{100} = \underline{\underline{0.02 \text{ sec.}}}$$

$$t_{V_{\max}} = 0.02 \text{ sec.}$$

$$\begin{aligned} \Rightarrow V_{\max} &= 50 \times 10^{-3} (80 e^{-100t} - 8000t e^{-100t}) \Big|_{t=0.02} \\ &= -0.541 \Rightarrow |V_{\max}| = \underline{\underline{0.541 \text{ V}}} \end{aligned}$$

14.

(9)

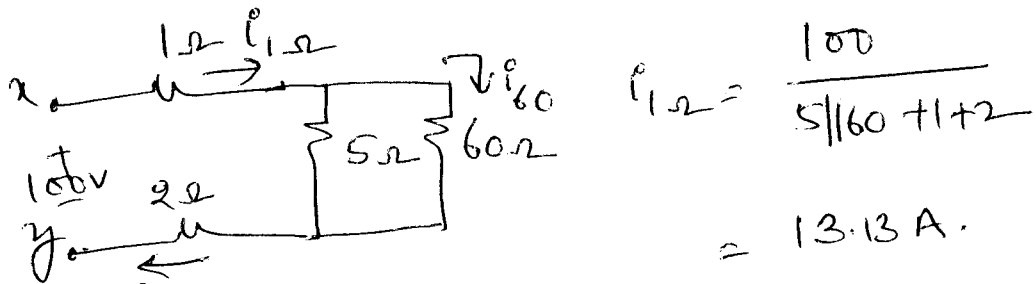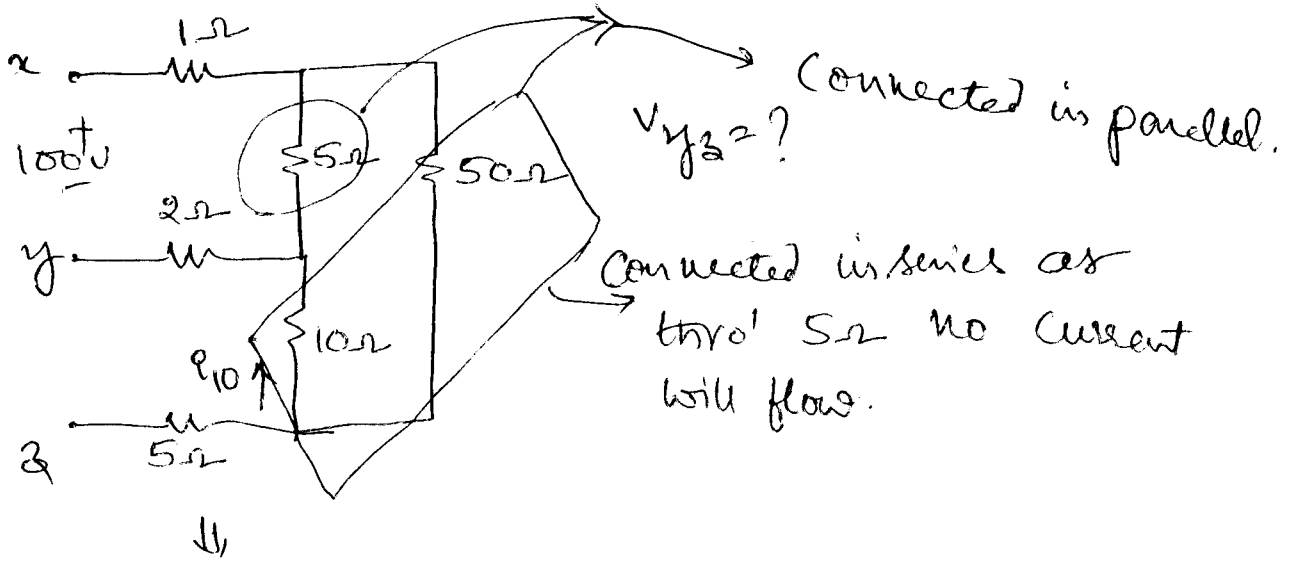


$$i_{1\Omega} = \frac{100}{5 \parallel 60 + 1 + 2} = 13.13 \text{ A.}$$

$$i_{60\Omega} = \frac{i_1 \times 5}{5 + 60} = 1.0101 \text{ A.}$$

$$i_{2\Omega} = i_{1\Omega} = 13.13 \text{ A.}$$

$$\Rightarrow i_{10} = 1.0101 \text{ A.}$$

⇒ Ckt will be come

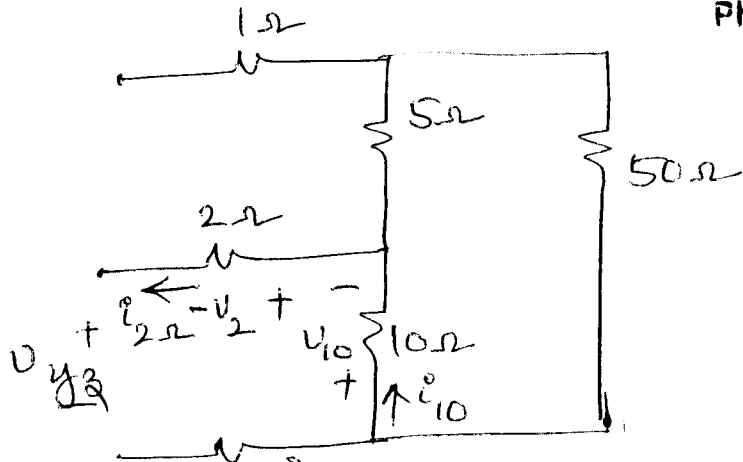


Applying KVL thro' V_{yz} , V_2 & V_{10}

$$V_{yz} = -V_2 - V_{10} = -2 \times i_{2\Omega} - 10 \times i_{10} = -36.361 \text{ V.}$$






Institute of Engineering Studies (IES)
 # 56, 2nd floor, behind Namura hotel
 22nd Main, Marenahalli, J.P. Nagar
 2nd Phase, Bangalore-560 078
 Ph: 080 32491693/9741900225

15.

Req. \Rightarrow

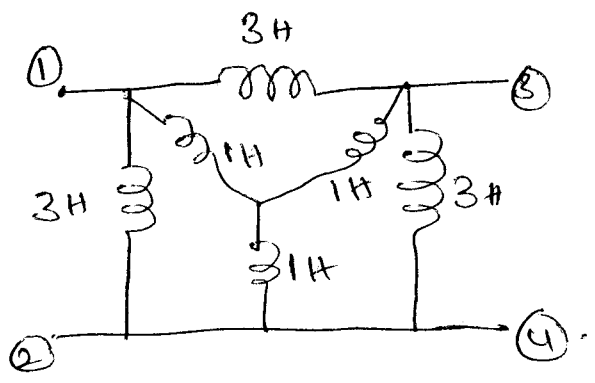

Convert Δ to Δ

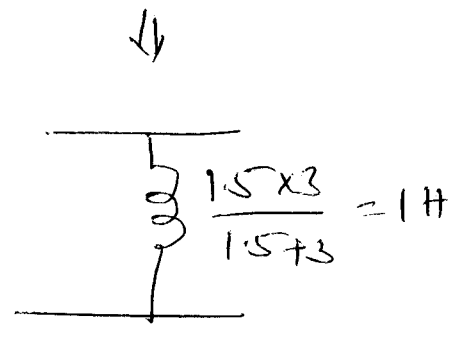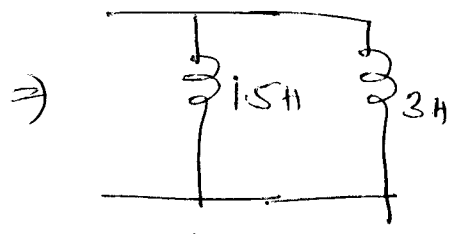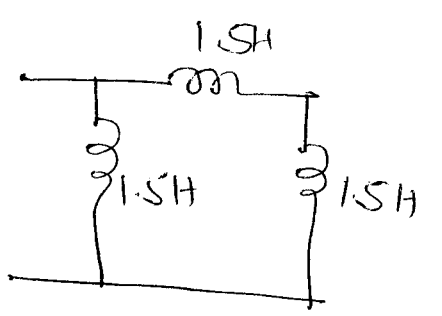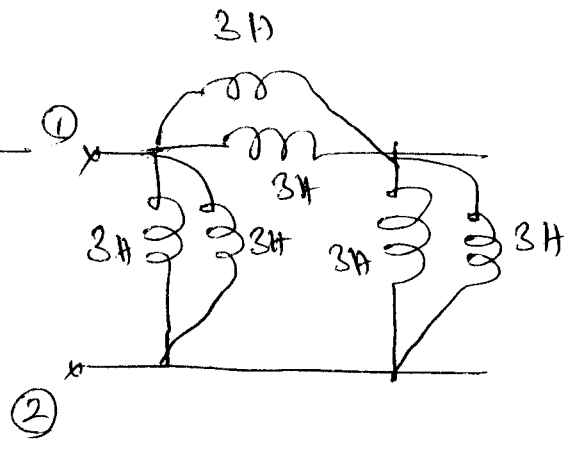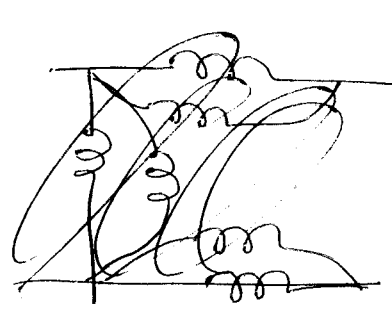

\Rightarrow Req. 1H

Institute of Engineering Studies (IES)

56, 2nd floor, behind Namura hotel
22nd Main, Marenahalli, J.P. Nagar
2nd Phase, Bangalore-560 073
Ph: 080 32491693/9741900225