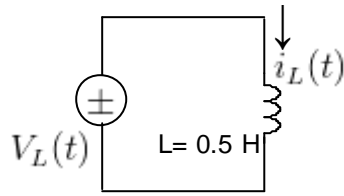


Institute of Engineering Studies (IES), Bangalore.


Practice paper on Network Analysis Transients.

1. For the circuit of figure, determine  $i_L(0)$  and  $i_L(t)$  for  $t \geq 0$  when  $V_L(t) = e^{-|t|}$  V



Ans: ,  $i_L(0) = 2A$ ,  $i_L(t) = 4 - 2 e^{-t}$  A

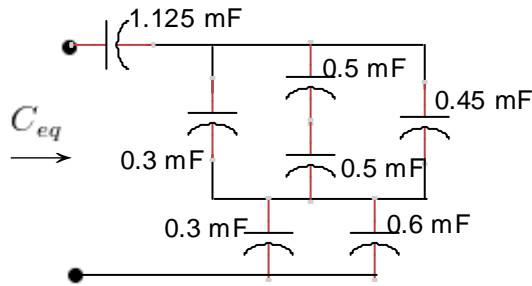2. For the circuit of figure, compute the equivalent capacitance  $C_{eq}$




Ans :  $C_{eq} = \frac{1}{3} mF$

3.(a) For  $i_s(t) = \sin(1000 t)$  mA in figure, calculate and sketch  $i_{out}(t)$  for  $0 \leq t \leq 15$  ms, assuming both inductor currents are zero at  $t=0$

(b) What is the instantaneous power delivered by the dependent source ?

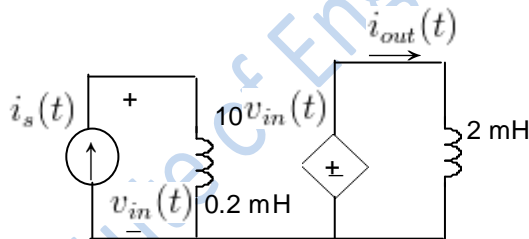(c) compute and sketch the energy stored in the 2 –mH inductor for  $0 \leq t \leq 15$  ms




Ans : (a)  $\sin(1000 t)$  mA;  $\sin^2(1000t)$  nW

4. In the circuit of figure, suppose  $i_s(t) = 4 \sin(4t)$  A . Find  $i_c(t)$

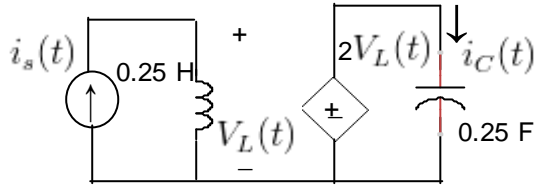
**Institute of Engineering Studies (IES), Bangalore.**

Practice paper on Network Analysis Transients.




Ans :  $8 \sin(4t)$  A

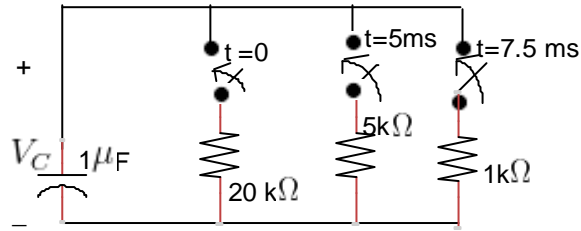
5. For the circuit of figure find an expression for  $V_C(t)$  using step functions assuming  $V_C(0) = 10$  V. plot this expression for  $0 \leq t \leq 12$  ms



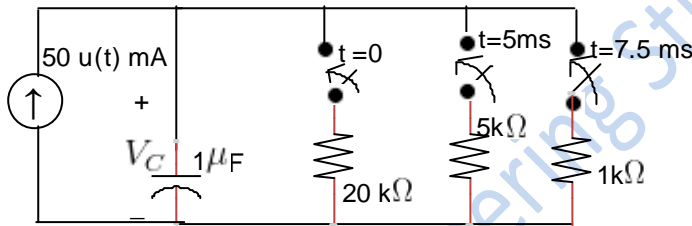6. For the circuit of figure, find an expression for  $V_C(t)$  using step functions assuming  $V_C(0^-) = 0$ . Plot this expression using for  $0 \leq t \leq 12$  ms



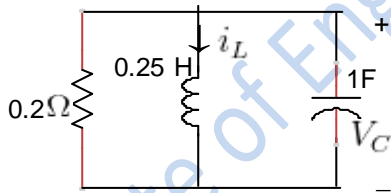7. Figure shows an over damped source-free circuit



(a) If  $V_C(0) = -1$  V and  $i_L(0) = 5$  A, find  $V_C(t)$  for  $t \geq 0$ . Plot the  $V_C(t)$  waveform and verify that there is no zero crossing


(b) If  $V_C(0) = -1$  V and  $i_L(0) = 5$  A, find  $V_C(t)$  for  $t \geq 0$ . Plot the  $V_C(t)$  waveform and verify that there is one zero crossing

8. In figure, the switch S has been at position A for a long time and is moved to position B at  $t = 0$

a. Find  $V_C(t)$  for  $t > 0$       b. Find  $i_L(0^+)$ ,  $i_L(\infty)$ , and  $i_L(t)$  for  $t > 0$

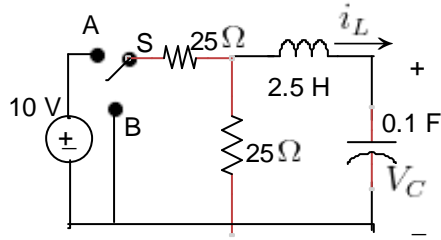
**Institute of Engineering Studies (IES), Bangalore.**

Practice paper on Network Analysis Transients.




9.(a) Find the value of  $R$  ( in ohms ) that makes the circuit of figure critically damped

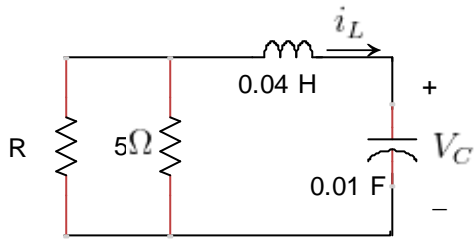
(b) Given this value of  $R$ , suppose  $V_C(0) = 5$  V and  $i_L(0) = -5$  A. Compute  $V_C(t)$  and determine the first time at which the capacitor voltage is zero. Plot your result to verify your calculation



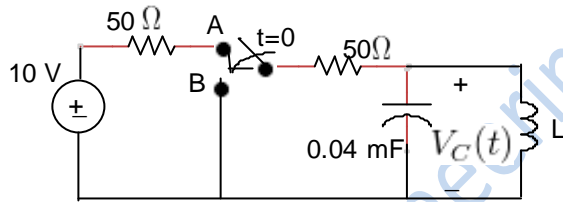10. The switch in the circuit of figure is in position A for a long time and moves to position B at  $t=0$ . Find the voltage  $V_C(t)$  for  $t > 0$  when  $L$  equals (a) 0.625 H, (b) 0.4 H, and (c) 0.2 H



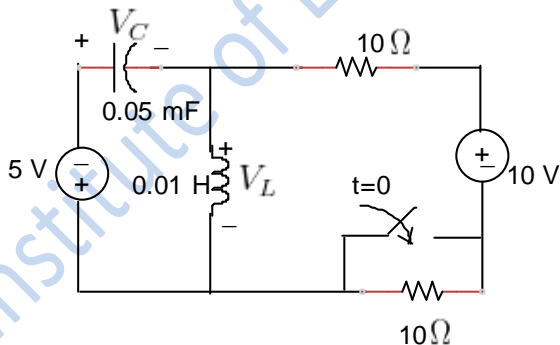
11. The circuit of figure is in the steady state with the switch open. The switch closes at  $t=0$ . Find  $V_L(t)$  and  $V_C(t)$  for  $t > 0$



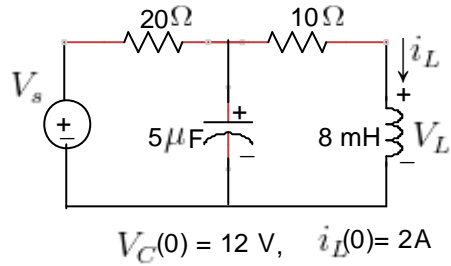12. Draw the exact dual of the circuit shown in figure. Specify the dual variables and the dual initial conditions. (b) write nodal equations for the dual circuit. (c) Write mesh equations for the dual circuit


Institute of Engineering Studies (IES), Bangalore.

Practice paper on Network Analysis Transients.




Ans : (a)  $V_{20}$ ,  $i_L$ ,  $i_C$  and  $V_C$ ;  $i_L(0) = 12 \text{ A}$  and  $V_C(0) = 2 \text{ V}$

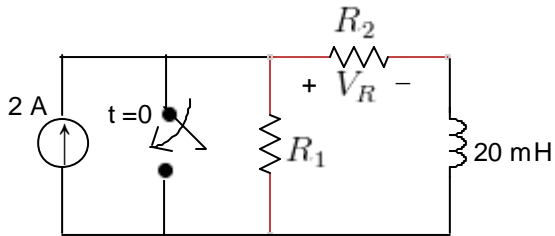13. Select values for  $R_1$  and  $R_2$  in the circuit of figure so that  $V_R(0^+) = 10 \text{ V}$  and  $V_R(1 \text{ ms}) = 5 \text{ V}$




Ans:  $R_1 = 7.82 \Omega$ ,  $R_2 = 13.86 \Omega$

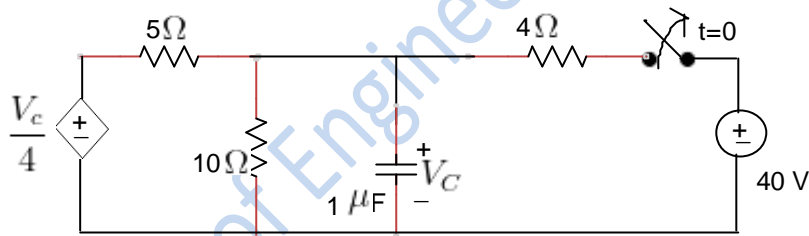14. Assume that the circuit shown in figure has been in the form shown for a very long time. Find  $V_C(t)$  for all  $t$  after the switch opens



Ans:  $20 e^{-250,000t} \text{ V}$

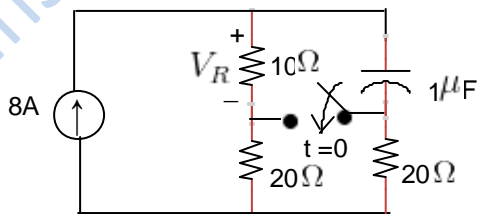15. In the circuit of figure, find  $V_R(t)$  for (a)  $t < 0$ ; (b)  $t > 0$ . Now assume that the switch has been closed for a very long time and opens at  $t = 0$ . Find  $V_R(t)$  for (c)  $t < 0$ ; (d)  $t > 0$



Institute of Engineering Studies (IES), Bangalore.

Practice paper on Network Analysis Transients.

Ans : (a) 80 V; (b)  $80 + 160 e^{-100,000t}$  V; (c) 80 V; (d)  $80 - 32 e^{-20,000t}$  V

Institute of Engineering Studies (IES), Bangalore