

# Pulse & Digital Circuits Practice Paper - I,

## (On Linear wave Shaping)

- ① A d.c voltmeter indicates 1.5V when measuring a square wave with a peak-to-peak amplitude of 5V. Calculate the positive and negative peak amplitudes of the square wave.

Ans : positive peak amplitude = 4V, and  
negative peak amplitude = -1V

- ② Determine the highest harmonic at the output of an amplifier which has an upper cut-off frequency of 1MHz  
(a) when a 10kHz square wave is applied as input and  
(b) when the input is a 150 kHz square wave.

Ans : (a) 100th (b) 6th

- ③ A 1kHz square wave having zero rise time and zero tilt is applied to an amplifier and is reproduced with  $t_r = 350\text{ns}$  and tilt = 5%. Determine the upper and lower 3-dB frequencies of the amplifier.

Ans :  $f_1 = 15.9155\text{Hz}$  ;  $f_2 = 1\text{MHz}$

- ④ Calculate the lowest square wave frequency that can be passed by an amplifier with a lower cut-off frequency of 1Hz if the output tilt is not to exceed 1%.

Ans : 0.1416 Hz

- ⑤ An amplifier has a bandwidth extending from 10Hz to 50kHz. Calculate the rise time and tilt that may be expected on the output when a 5kHz square wave is applied as input.

Ans :  $t_r = 7\mu\text{s}$  ; % tilt = 0.2832%

- ⑥ A 10V step is switched on to a 22k $\Omega$  resistor in series with a 30pF capacitor. Calculate the rise time of the capacitor voltage, the time required for the capacitor to charge to 63.2% of its maximum charge, and the time for the capacitor to become completely charged.

Ans:  $14.52 \mu s$ ,  $6.6 \mu s$ ,  $33 \mu s$

⑦ A 5V pulse with a width of  $100 \mu s$  is applied to a series RC circuit with  $R = 27 k\Omega$  and  $C = 0.1 \mu F$ . Determine the amplitude of  $e_c$  at the end of the pulse.


Ans:  $0.1818 \text{ Volt}$ .

⑧ An amplifier has an input coupling capacitor of  $30 \mu F$  and an input resistance of  $20 k\Omega$ . Determine the lowest square wave frequency that can be applied as an input, if the output tilt is not to exceed 5%. (Ans:  $16.67 \text{ Hz}$ )

⑨ An oscilloscope displays a  $5 \text{ Hz}$  square wave form with a 6% tilt. The signal input has no tilt and is coupled to the oscilloscope via a  $4.7 \mu F$  capacitor. Calculate the oscilloscope input resistance.

Ans:  $354.61 k\Omega$  (or)  $0.35461 M\Omega$

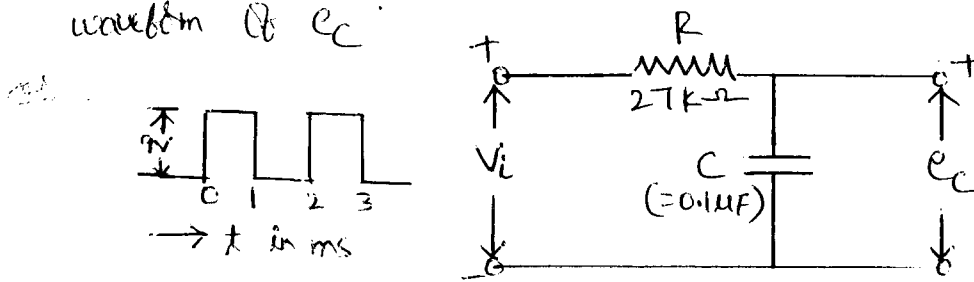⑩ For the circuit and input shown in the figure, determine  $e_c$  at  $t = 2.5 \text{ ms}$  and sketch the output waveform. Also sketch the settled waveform of  $e_c$ .



Ans: At  $t = 2.5 \text{ ms}$ ,  
 $e_c = 3.1198 \text{ mV}$

⑪ A square wave whose peak-to-peak value is 1 volt extends  $\pm 0.5 \text{ V}$  with respect to ground. The duration of the positive section is  $0.1 \text{ sec}$  and of the negative section is  $0.2 \text{ sec}$ . If this waveform is impressed upon an RC differentiating circuit whose time constant is  $0.2 \text{ sec}$ , what are the steady state maximum and minimum values of the output waveform?

Ans: Max. value  $V_1 = 0.81368 \text{ V}$   
Min. value  $V_2 = -0.50647 \text{ V}$

(12) A 10Hz symmetrical square wave whose peak-to-peak amplitude is 2V is impressed upon a high pass circuit whose lower 3-dB frequency is 5Hz. Calculate and sketch the output waveform. In particular, what is the peak-to-peak amplitude? (Ans: 3.3116V)

(13) An RC differentiated circuit is driven from a 500Hz symmetrical square wave of 10V peak-to-peak. Calculate and sketch the output voltage under steady state if  $RC = 1 \text{ msec}$ . Sketch also the input on the same time axis. Ans: (2.6895Vdt, -2.6895Vdt)

(14) A 1KHz symmetrical square wave of  $\pm 10\text{V}$  is applied to an RC circuit having 1ms time constant. Calculate and plot the output for the RC configuration as (a) high pass circuit (b) low pass circuit. Ans: (a) +7.5508 volts (b) +2.45 volts.

(15) A symmetrical square wave whose average value is zero has a peak-to-peak amplitude of 20 volts and a period of 2msec. This waveform is applied to a low pass circuit whose upper 3-dB frequency is  $1/2\pi \text{ MHz}$ . Calculate and sketch the steady-state waveform. In particular, what is the peak-to-peak output amplitude? Ans: 4.6212 volt

(16) The ramp shown in the figure is applied to a RC high pass circuit. Draw to scale the output waveform for the following cases  
(a)  $T = 0.2 RC$  and (b)  $T = 10 RC$

Ans: (a)  $0.90635 \Delta T$  (b)  $0.1 \Delta T$

(17) A pulse of 5V amplitude and duration 0.5 msec. is applied to a RC high pass circuit with  $R = 22 \text{ k}\Omega$  and  $C = 0.47 \mu\text{F}$ . Sketch the output waveform and determine the percentage tilt in the output.

Ans: % tilt = 4.7206%

**Institute of Engineering Studies (IES)**



# 56, 2nd floor, behind Namura hotel

22nd Main, Marenahalli, J.P. Nagar

2nd Phase, Bangalore-560 074

Ph: 080 32491693/97419000

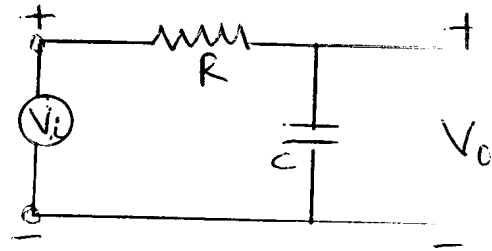
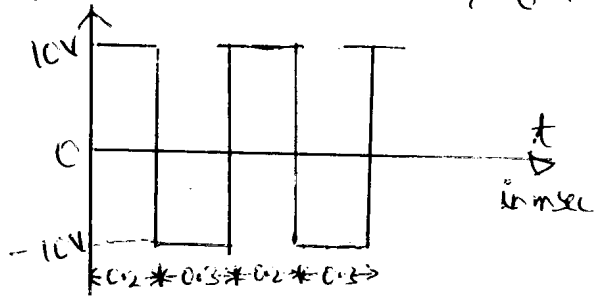
- (18) The input waveform shown in figure is applied to a LP RC circuit at  $t=0$ . Sketch the output voltage waveform starting from  $t=0$  to  $t=1\text{ms}$ . The circuit uses  $R = 100\ \Omega$ ,  $C = 0.1\ \mu\text{F}$ . The input signal source resistance =  $1\ \text{k}\Omega$ . Assume initial capacitor voltage is zero. (Ans:  $6.7536\ \text{V}$ ,  $6.93142\ \text{V}$ ,  $-8.9044\ \text{V}$ ,  $-8.89273\ \text{V}$ ).



- (19) A Symmetrical Square wave of  $\pm 5\ \text{V}$  at a frequency of  $5\ \text{kHz}$  is applied to a HP RC circuit with a cut-off frequency of  $20\ \text{kHz}$ . Sketch the steady-state input and output voltage waveforms. Calculate the steady state output voltage levels (Ans:  $10\ \text{V}$ ,  $0\ \text{V}$ )

- (20) The pulse from a high voltage generator (a magnetron) rises linearly for  $0.05\ \mu\text{sec}$  and then remains constant for  $1\ \mu\text{sec}$ . The rate of rise of the pulse is measured with a RC differentiating circuit whose time-constant is  $250\ \text{psec}$ . If the positive output voltage from the differentiator has a maximum value of  $50\ \text{V}$ , what is the peak voltage of the generator? (10kV)

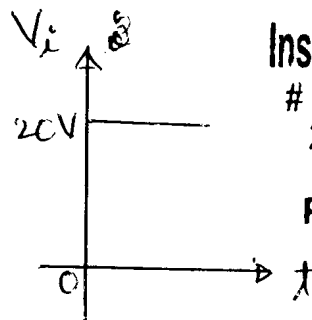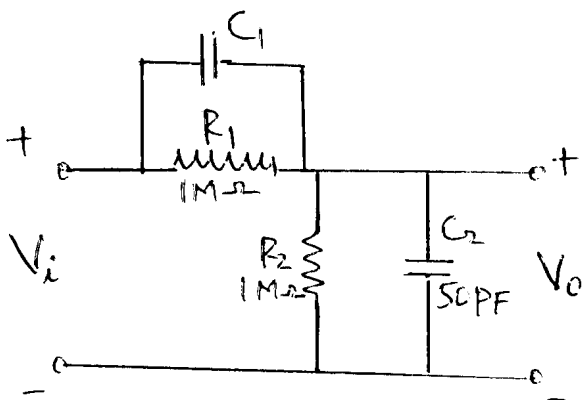- (21) Compute and draw to scale the output waveform for  $C_1 = 50\ \text{PF}$ ,  $C_1 = 75\ \text{PF}$  and  $C_1 = 25\ \text{PF}$ . The input is a  $20\ \text{V}$  step.



**Institute of Engineering Studies (IES)**

# 56, 2nd floor, behind Namura hotel


22nd Main, Marenahalli, J.P. Nagar

2nd Phase, Bangalore-560 078


Ph: 080 32491693/9741900225

- Ans: (a) when  $C_1 = 50\ \text{PF}$ ,  $V_0(\infty) = V_0(0^+) = 10\ \text{V}$ , (b)  $C_1 = 75\ \mu\text{F}$ ,  $V_0 = 12\ \text{V}$   
 (c) when  $C_1 = 25\ \text{PF}$ ,  $V_0(\infty) = V_0(0^+) = 6.6667\ \text{V}$

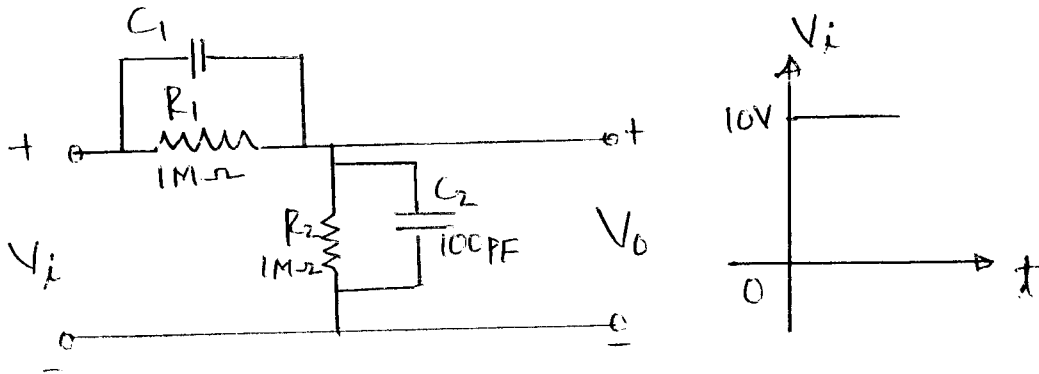- 22) For the attenuator circuit shown in the figure, calculate and plot to scale the output for the cases (a)  $C_1 = 50 \text{ pF}$  and (b)  $C_1 = 150 \text{ pF}$ . The input  $V_i$  is a step of  $10 \text{ V}$ . (Ans: (a)  $5 \text{ V}$ , (b)  $5 \text{ V}$ )



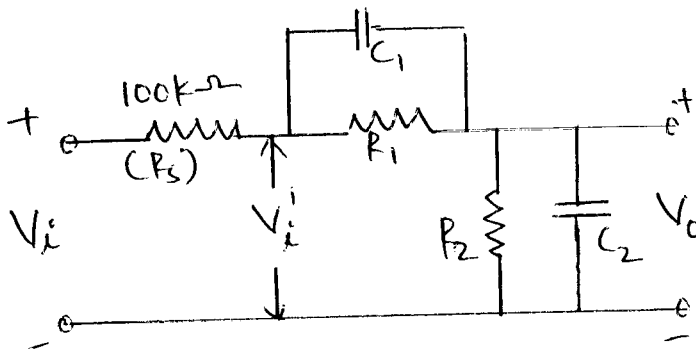- 23) The input  $V_i$  in the circuit shown is a  $20 \text{ V}$  step. Calculate and plot to scale the output voltage.




$$C_1 = C_2 = 50 \text{ pF}$$

$$R_1 = R_2 = 1 \text{ M}\Omega$$

$$V_i = 20 \text{ V step}$$

Ans: (a) at  $t = 0^+$ ,  $V_c = 0$ , (b)  $t = \infty$ ,  $V_R = 19.04762 \text{ Volt}$ .

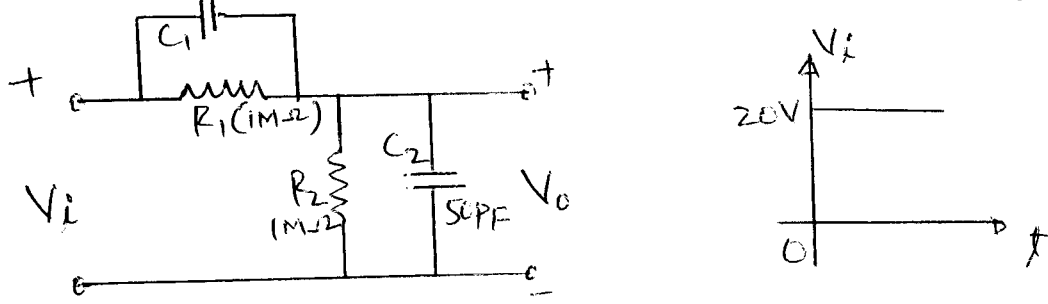- 24) Compute and draw to scale the output waveform for  $C = 50 \text{ pF}$ ,  $C = 75 \text{ pF}$ , and  $C = 25 \text{ pF}$ , if the input is a  $20 \text{ V}$  step for the following circuit.



- 25) The pulse from a high voltage generator (a magnetron) rises linearly for  $0.05 \mu\text{sec}$  and then remains constant for  $1 \mu\text{sec}$ . The rate of rise of the pulse is measured with an RC differentiating circuit whose time-constant is  $250 \text{ psec}$ . If the positive output voltage from the differentiator has a max. value of  $50 \text{ V}$ , what is the peak voltage of the generator?

(26) An ideal 1 msec pulse is fed to a low-pass circuit. Calculate and plot the output waveform under the following conditions: The 3dB frequency is (a) 10 MHz (b) 1 MHz (c) 0.1 MHz

Ans: (a)  $V_o = V$  (b)  $V_o = 0.98V$  (c)  $V_o = 0.46642V$ .

(27) A 10 Hz square wave is fed to an amplifier. Calculate and plot the output waveform under the following conditions: The lower 3dB frequency is (a) 0.3 Hz (b) 3 Hz (c) 30 Hz


Ans: (a)  $V_o = 0.4764V$  (b)  $T = 0.0531\text{sec}$  (c)  $0.0053\text{sec}$

(28) A symmetrical square wave whose peak-to-peak amplitude is 2V and whose average value is zero is applied to a RC integrating circuit. The time constant is half the period of the square wave. Find the peak-to-peak value of the output voltage. (Ans: 0.9242V)

(29) A square wave whose peak-to-peak amplitude is 2V extends  $\pm 1V$  with respect to ground. The duration of the positive section is 0.1 sec and that of the negative section is 0.2 sec. If this waveform is impressed upon a RC integrating circuit whose time constant is 0.2 s, what are the steady state max. and min. values of the output waveform?

Ans: -0.6273 Volt, 0.01298 Volt.

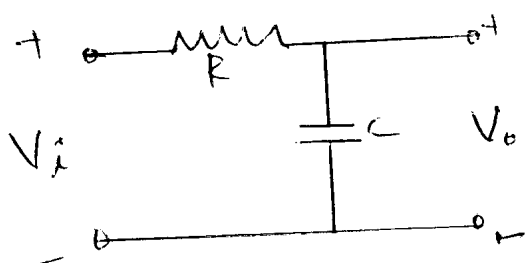(30) Prove that an RC circuit behaves as a reasonably good integrator, if  $RC \gg T$ , where  $T$  is the period of an input sinusoid  $E_m \sin \omega t$ .



**Institute of Engineering Studies (IES)**

# 56, 2nd floor, behind Namura hotel

22nd Main, Marenahalli, J.P. Nagar

2nd Phase, Bangalore-560 078

Ph: 080 32491693/9741900225